

Solar from Scratch Student Worksheet

duction: In your own words, describe how solar cells produce electricity.
,,
be for these cells wired in parallel? What if they were wired in series?
1

you can get a total voltage of 6V and 1.2A?
eriment:
Based on your ideas from the last question, wire a solar panel charger yourself! Sket your final design below. Hint: check that your voltage and current are what you want before connecting to your buck converter (see question 5).
Based on your ideas from the last question, wire a solar panel charger yourself! Sket your final design below. Hint: check that your voltage and current are what you want
Based on your ideas from the last question, wire a solar panel charger yourself! Sket your final design below. Hint: check that your voltage and current are what you want
Based on your ideas from the last question, wire a solar panel charger yourself! Sket your final design below. Hint: check that your voltage and current are what you want

II.

	Test your solar cell array using alligator clips and a multimeter. Note your values of DC voltage and current from each different configuration you try. Check in bright sunlight v regular classroom lighting. Are your voltage and/or current values different?
6.	What problems did you run into while trying to build your charger? What did you try to
	solve them? What worked and what didn't? How were you creative?
	solve them? What worked and what didn't? How were you creative?
	solve them? What worked and what didn't? How were you creative?
	solve them? What worked and what didn't? How were you creative?
	solve them? What worked and what didn't? How were you creative?
	solve them? What worked and what didn't? How were you creative?

Design a	 	Sketch your thoughts	or write notes

III. Discussion:

8.	You need to generate at least 1900 W of power for your home, which would be true if your household uses about 200 kWh per month (typical for a smaller home without lots of air conditioning and heating needs) and you live in Washington, which gets 3.57 peak sun hours in a day on a fixed solar panel. If you have solar cells that generate 5V and 1A during these peak sun hours, how many cells would you need? How would you wire them together? If the cells are about 10 in², how much roof area do you need?